

Faculty of Engineering, Environment and Computing
201CDE/5045CEM Analogue and Digital Electronics 2

Digital electronics coursework

Lecturer

Dr Server Kasap

Student:

Aziz Abdul

ID: 10289484

Traditional Design

Last digit of my student ID is 4 therefore this are the values I used:

$\epsilon_0 = "01"$, $50p = "10"$, $\epsilon_1 = "11"$, $\epsilon_2 = "00"$

state diagram:

6 States



state table:

state	next state				change	diff. prev. st.
	0 x=01	50 x=10	1 x=11	2 x=00		
a	a	c	f	b	01	0
b	f	f	f	f	11	0
c	c	f	d	e	01	0
d	f	f	f	f	10	0
e	d	d	d	d	11	0
f	a	a	a	a	01	1

0 = 01
 50 = 10
 1 = 11
 2 = 00

States:

a = 000
 b = 001
 c = 010
 d = 011
 e = 100
 f = 101
 g = 110
 h = 111

In total I was able to get an optimum number of 6 states to create the machine. Additional 2 states are created as don't care to fill and create 32 combinational lines in the transitional table

Transitional table

state	x	0	state	D_{x0}	D_{x1}	D_{x2}
000	01	010	000		000	
000	10	010	010		010	
000	11	010	101		101	
000	00	010	001		001	
001	01	110	101		101	
001	10	110	101		101	
001	11	110	101		101	
001	00	110	101		101	
010	01	010	010		010	
010	10	010	101		101	
010	11	010	011		011	
010	00	010	100		100	
011	01	100	101		101	
011	10	100	101		101	
011	11	100	101		101	
011	00	100	101		101	
100	01	110	011		011	
100	10	110	011		011	
100	11	110	011		011	
100	00	110	011		011	
101	01	011	000		000	
101	10	011	000		000	
101	11	011	000		000	
101	00	011	000		000	
110	01	010	---		---	
110	10	010	---		---	
110	11	010	---		---	
110	00	010	---		---	
111	01	010	---		---	
111	10	010	---		---	
111	11	010	---		---	
111	00	010	---		---	

d flip flop excitation table:

Q Output		Input
$Q_{(n)}$	$Q_{(n+1)}$	D_n
0	0	0
0	1	1
1	0	0
1	1	1

Kmaps:

Q_2, Q_1, Q_0 D_A

	000	001	011	010	100	101	111	110
00	0	1	1	1	0	0	X	X
01	0	1	1	0	0	0	X	X
11	1	1	1	0	0	0	X	X
10	0	1	1	1	0	0	X	X

5-variable Karnaugh map (overlay)

$$D_A = \overline{x_2} \overline{Q_0} Q_1 + \overline{Q_0} Q_2 + x_1 x_2 \overline{Q_1}$$

$\backslash q_0 q_1 q_2$ D_b

$x_1 x_2$	000	001	011	010	100	101	111	110
00	0	0	0	0	1	1	X	X
01	0	0	0	1	1	1	X	X
11	0	0	0	1	1	1	X	X
10	1	0	0	0	1	1	X	X

5-variable Karnaugh map (overlay)

$$D_b = q_0 \overline{q_2} + x_2 q_1 \overline{q_2} + x_1 \overline{x_2} \overline{q_1} \overline{q_2}$$

$\backslash q_0 q_1 q_2$ D_c

$x_1 x_2$	000	001	011	010	100	101	111	110
00	1	1	1	0	1	0	X	X
01	0	1	1	0	1	0	X	X
11	1	1	1	1	1	0	X	X
10	0	1	1	1	1	0	X	X

5-variable Karnaugh map (overlay)

$$D_c = \overline{x_1} \overline{x_2} \overline{Q_1} + \overline{Q_0} Q_2 + Q_0 \overline{Q_2} + x_1 \overline{Q_0} Q_1 + x_1 x_2 \overline{Q_0}$$

output function maps and logic equations:

change (coin out):

O1:

		$Q_1 Q_2$			
		00	01	11	10
Q_0	0	0	1	1	0
	1	1	0	0	0

$$O_1 = \overline{Q_0} Q_2 + Q_0 \overline{Q_1} \overline{Q_2}$$

O2:

		$Q_1 Q_2$			
		00	01	11	10
Q_0	0	1	1	0	1
	1	1	1	1	1


$$Q_2 = \overline{Q_0} \overline{Q_1} + \overline{Q_2} + Q_0 Q_1$$


Can out:

	$Q_1 Q_2$	00	01	11	10
Q_0	0	0	0	0	0
1	0	1	0	0	0


$$Can = Q_0 \overline{Q_1} Q_2$$


Multisim:

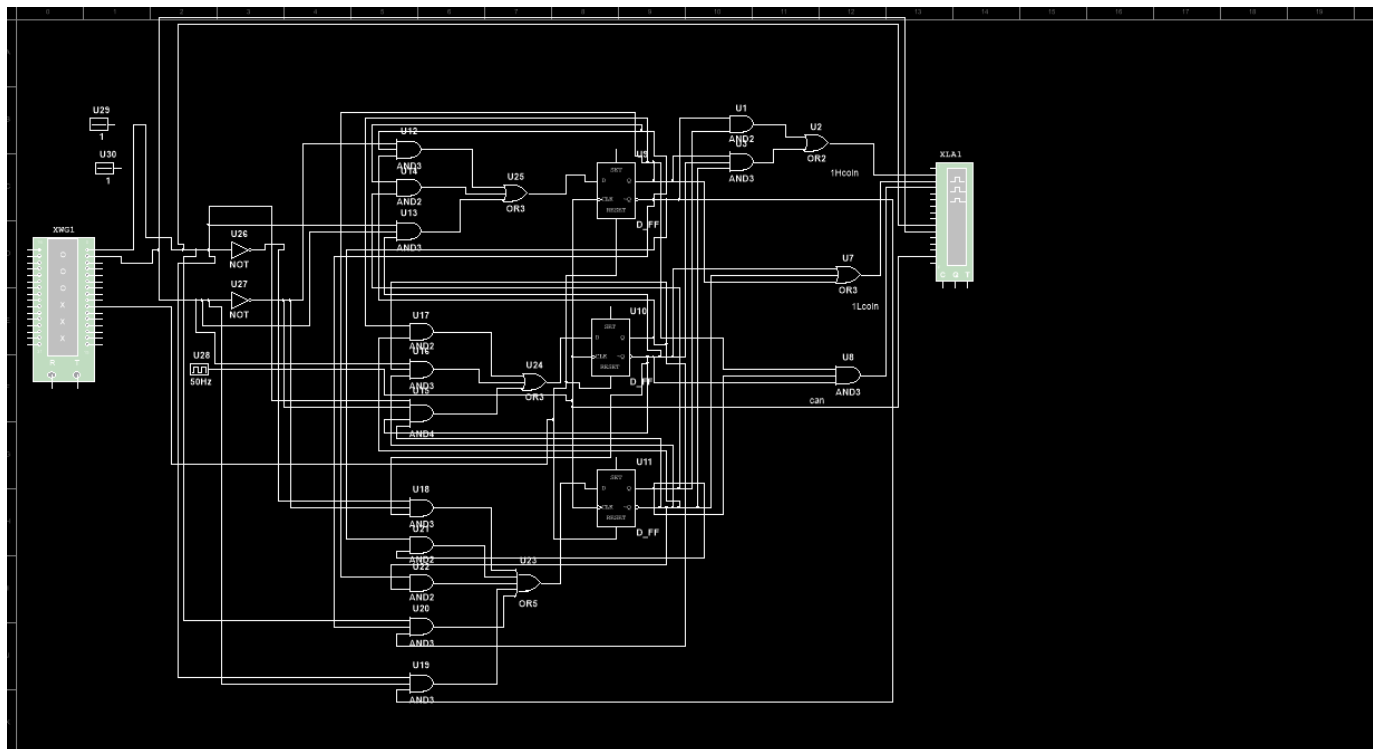

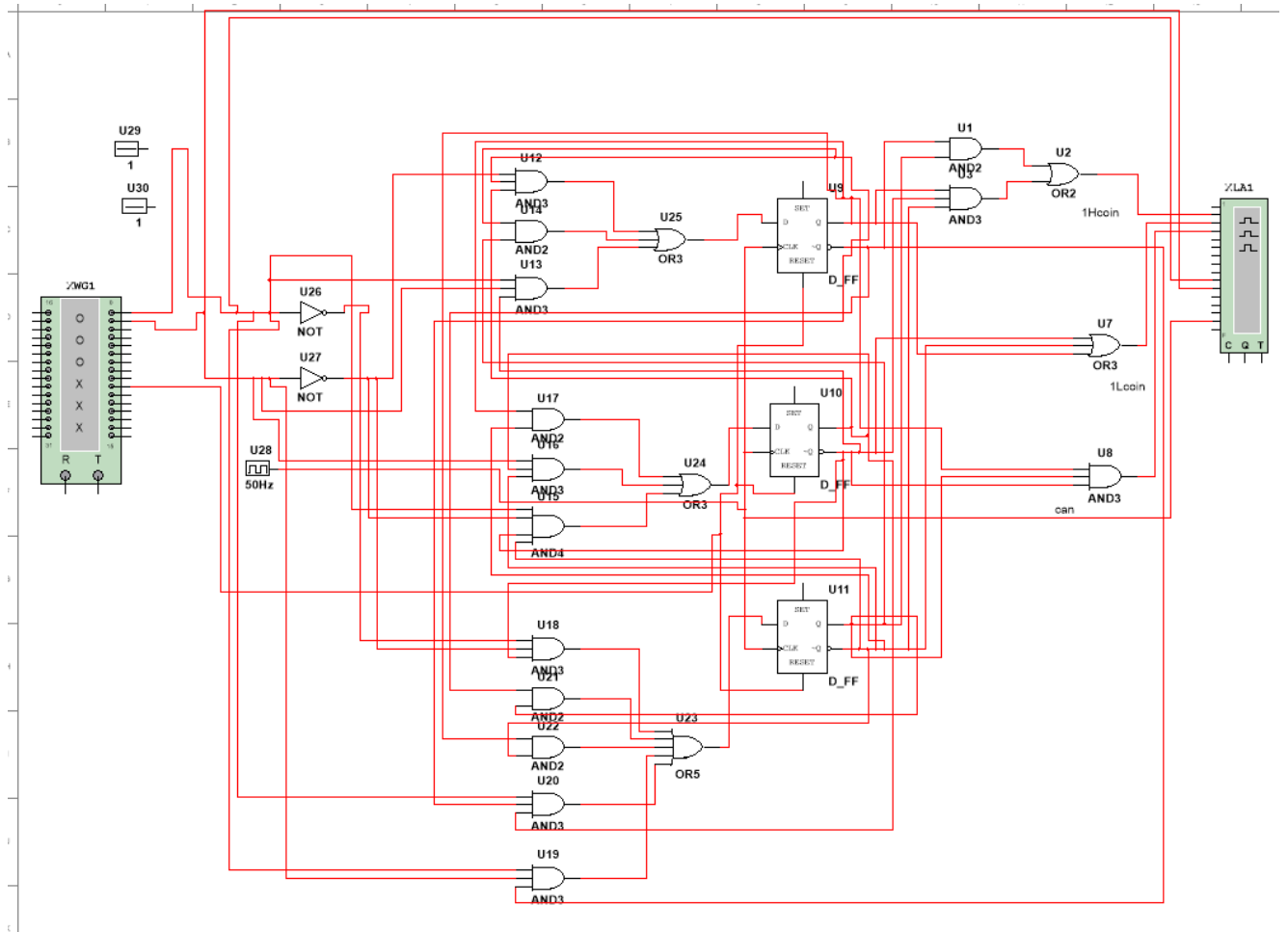


Proof of simulations:

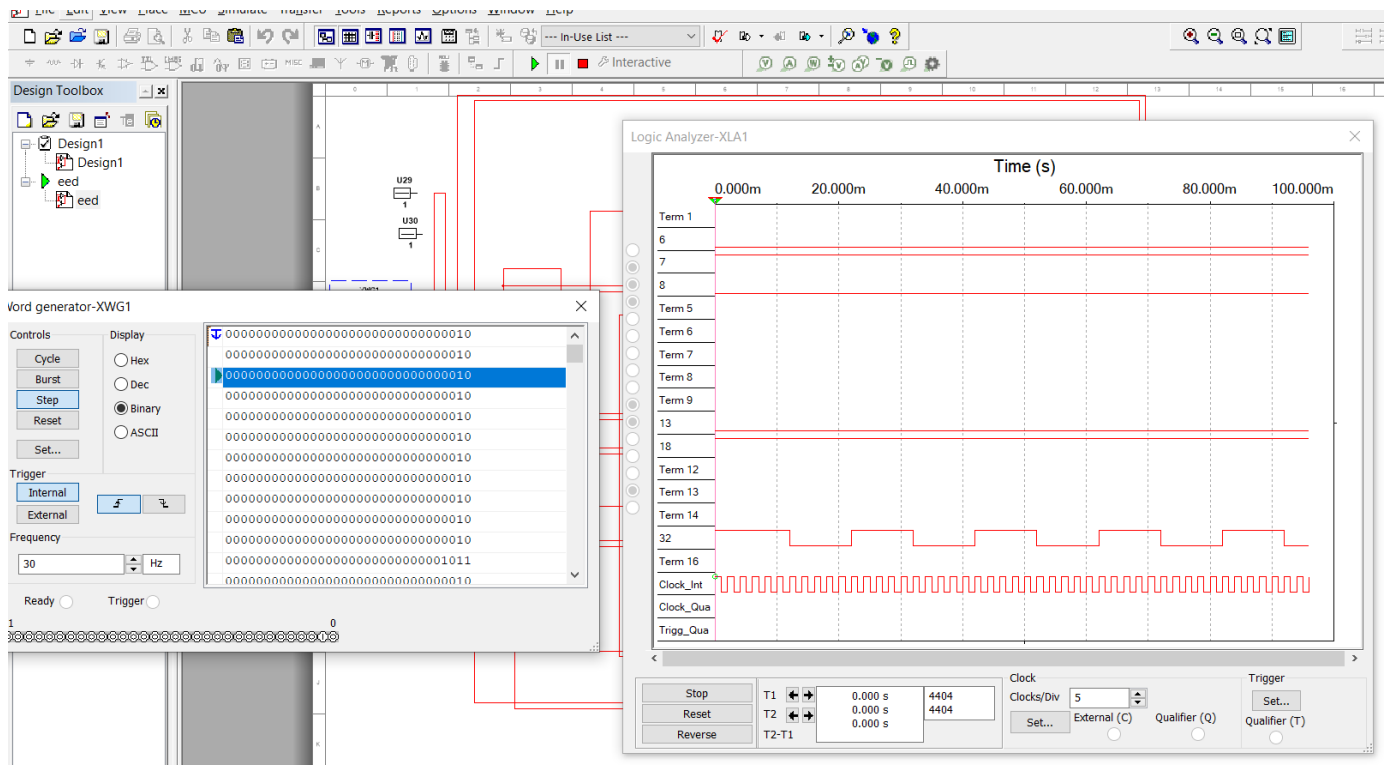

 


£0 case:

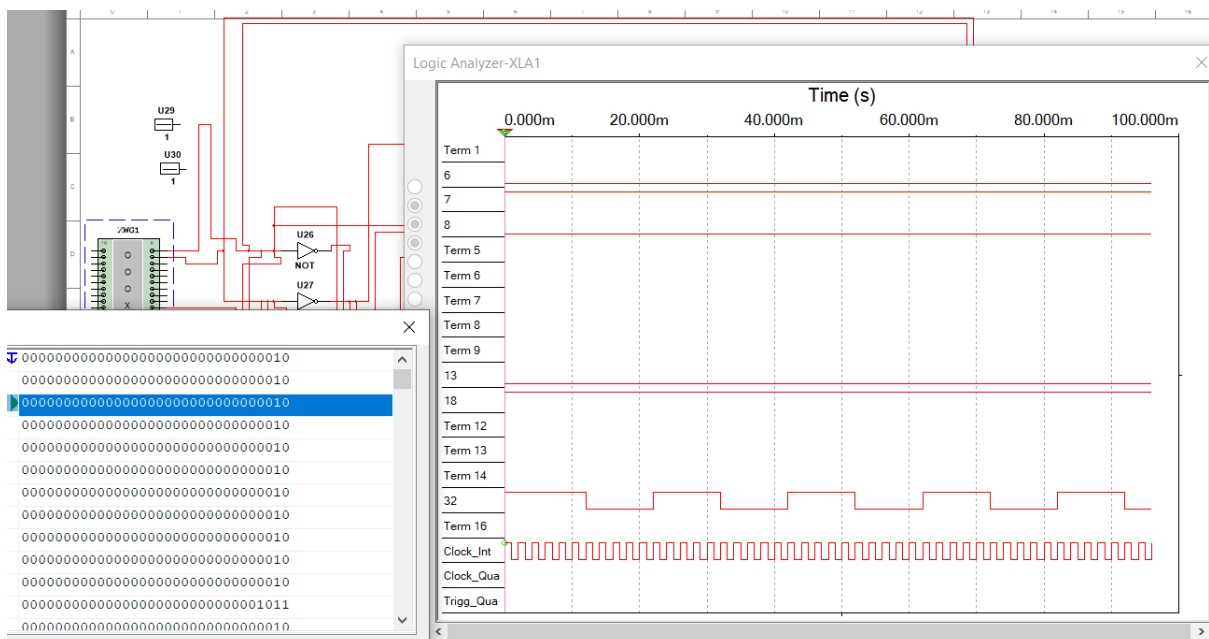

When coin entered is £0, signal 01 (corresponding to £0 for my case) is fed into the logic system. The input $X_1 = 0$ and input $X_0 = 1$ can be seen where, X_0


signal is high and X1 signal low. We get no change as it can be seen where output X1X2 = 01 corresponding to £0 change, no can is given (0 state). The output (changes) X1 is low and output X0 is high, representing 01.

£2 case:

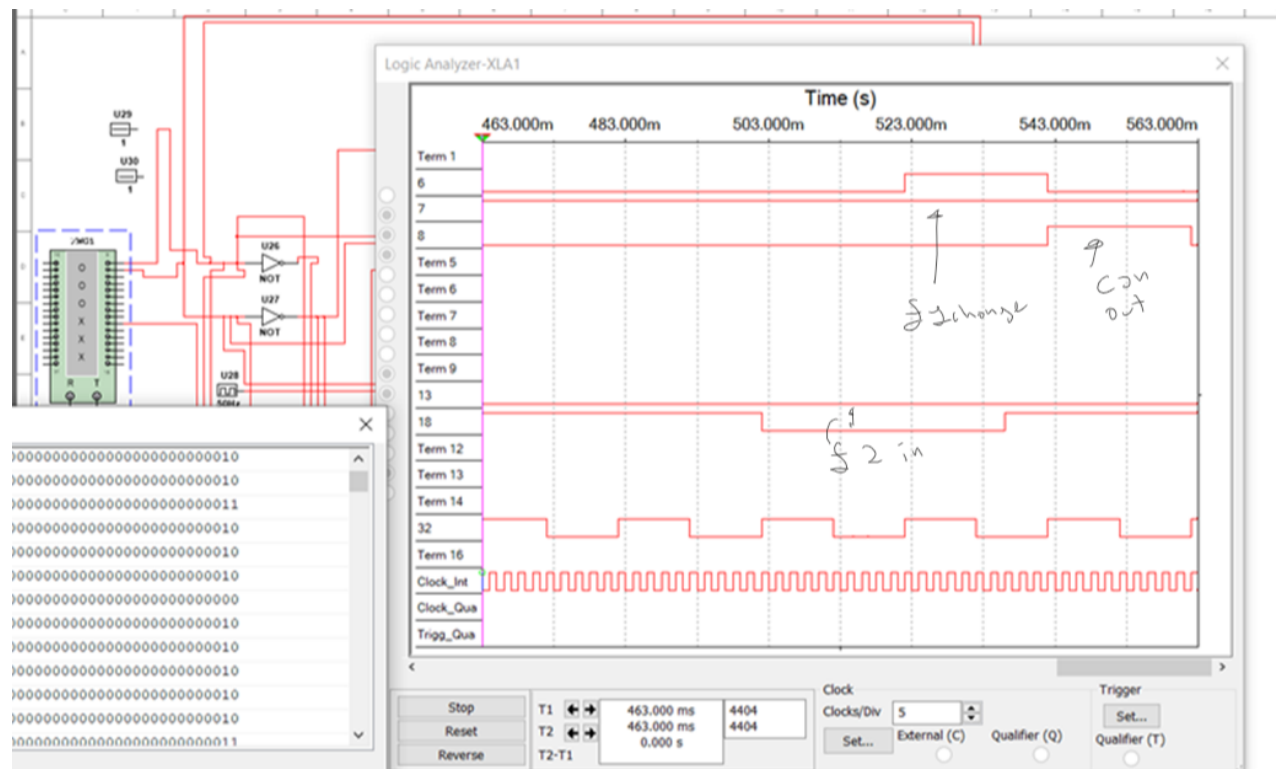


£2 pound is inserted into the machine by taking both inputs waves to 0. The machine then gives £1 change followed by a can.

50p and £2 case:

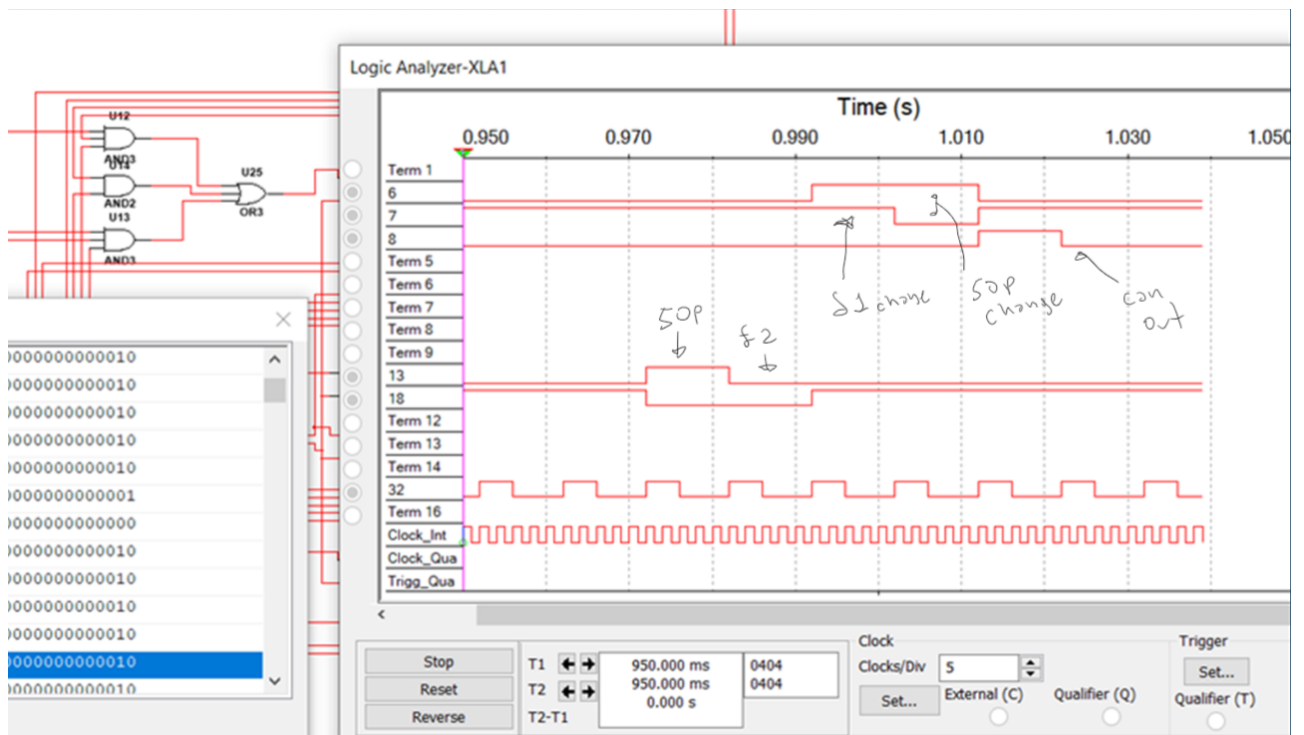


50p and 50p case:

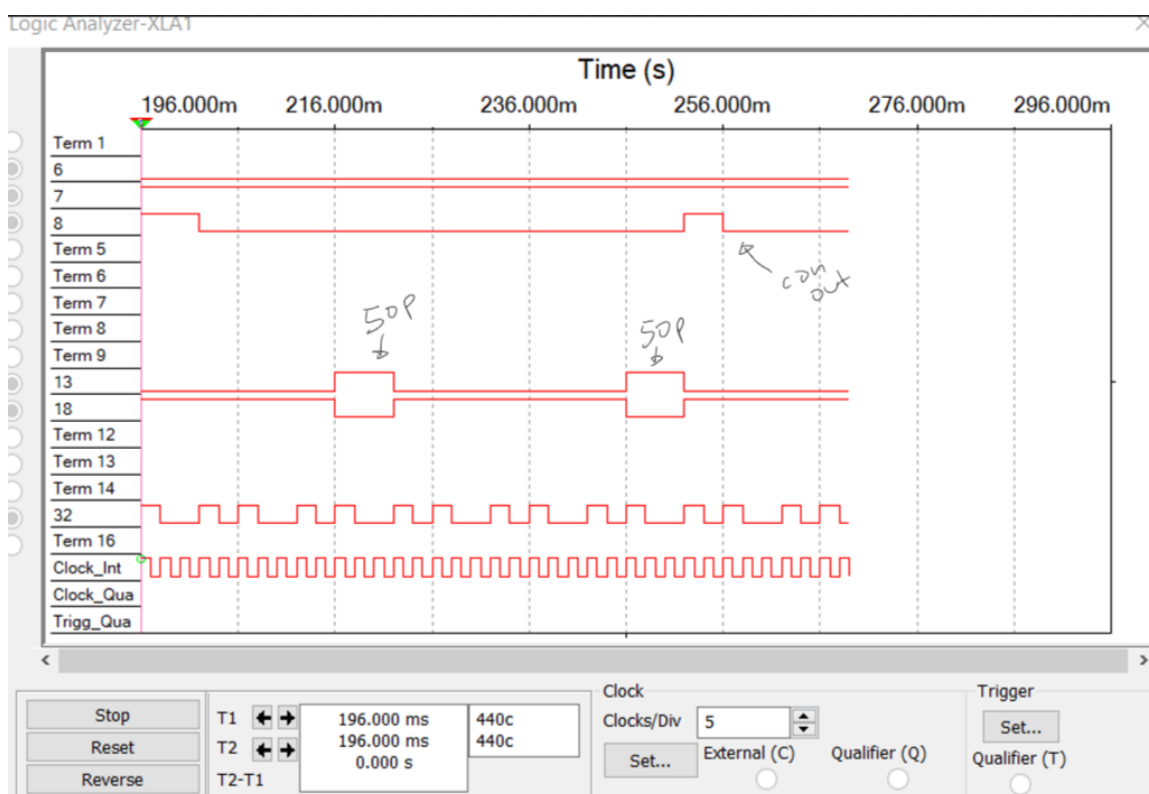


Two 50p inputs add up to £1 therefore a can is dispensed and no change is given.

£1 case:

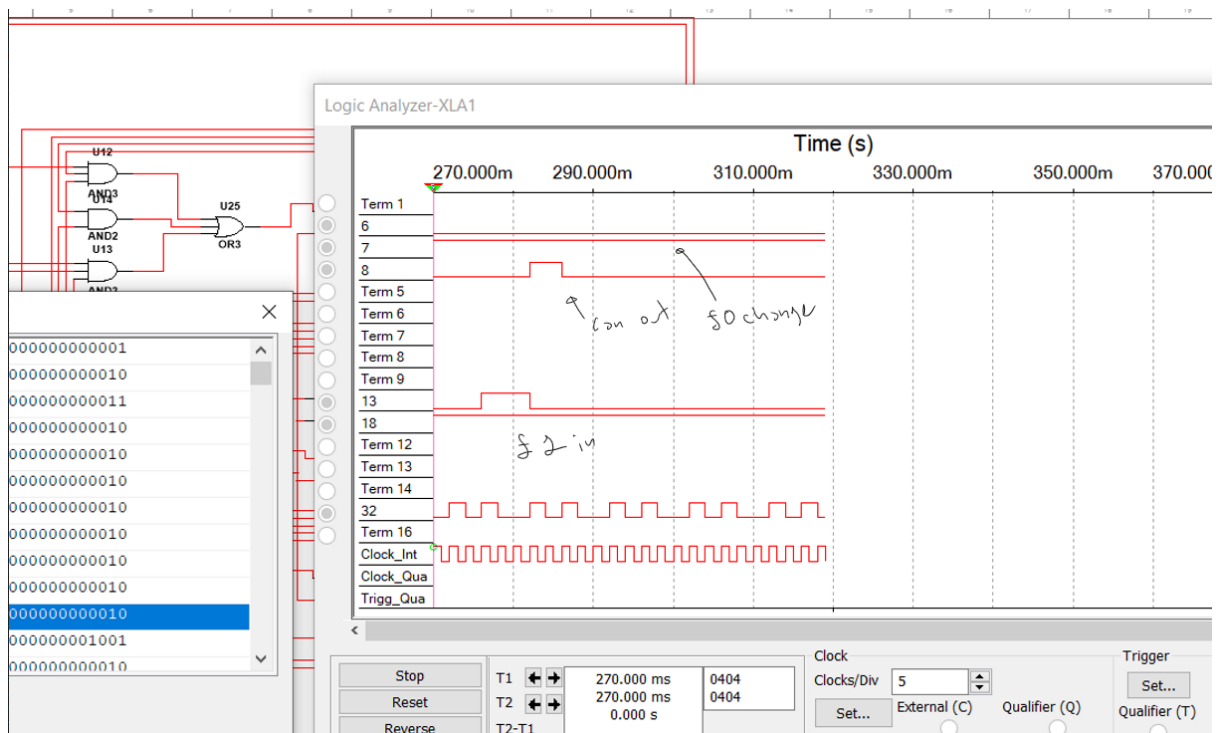


50p and £1 case:

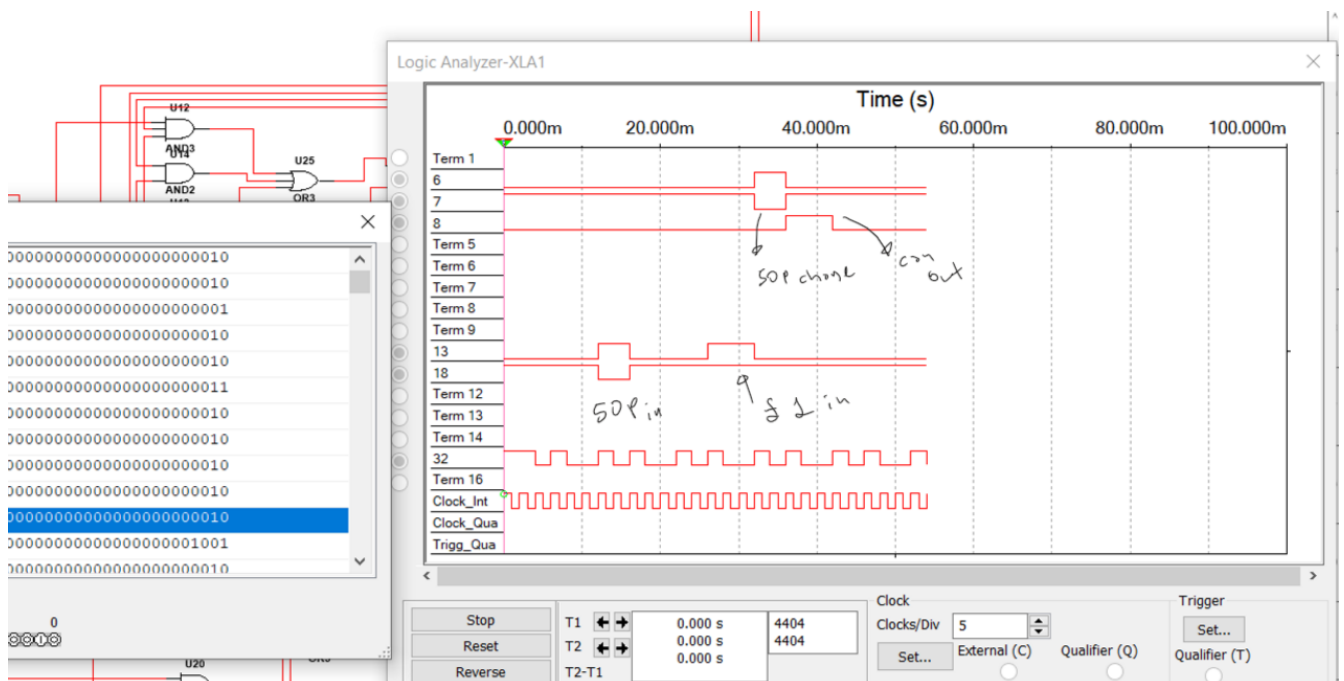


A issues that I encountered was that the memory stored the previous unused input value 50p, therefore when I add the next signal eg £1 pound I get £1.50 input in total therefore I get a wrong waveform. To overcome this issue the

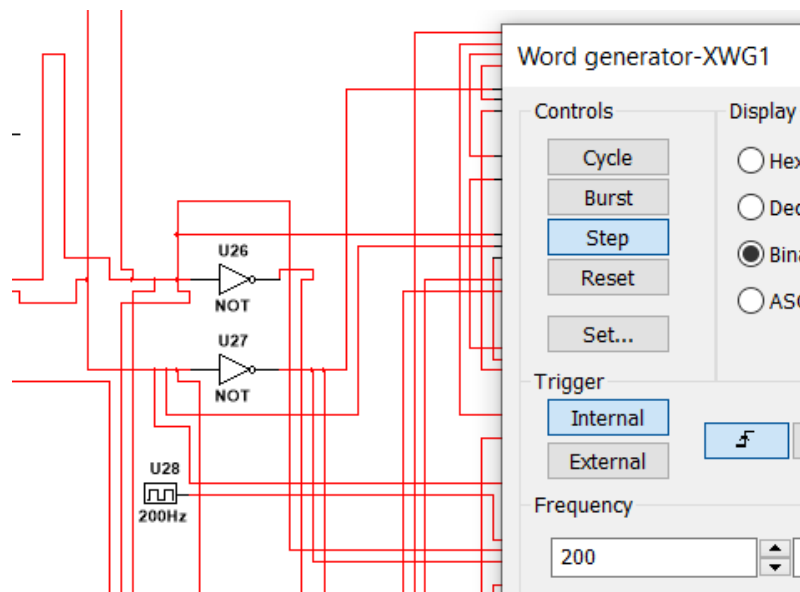simulation had to be restarted before each test to clean its memory. A simple fix was to add a reset option connected to three D flip flops, A little impulse in the beginning will clear the memory.



The clock frequency connected to D ff is selected to run at 200Hz

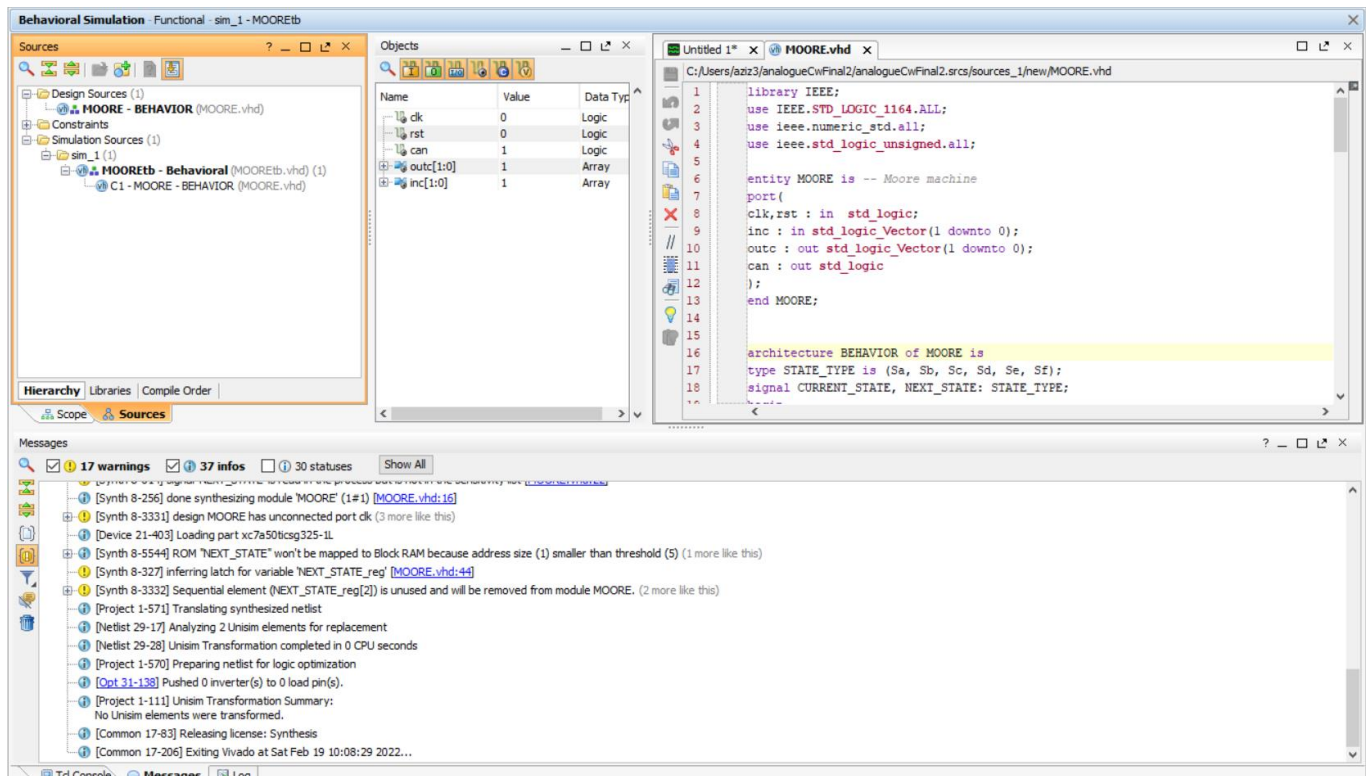VHDL model design with proof of compilation:



VHDL model code:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use ieee.numeric_std.all;

use ieee.std_logic_unsigned.all;

entity MOORE is -- Moore machine

port(

clk,rst : in std_logic;

inc : in std_logic_vector(1 downto 0);

outc : out std_logic_vector(1 downto 0);

can : out std_logic

);

end MOORE;

architecture BEHAVIOR of MOORE is

```

type STATE_TYPE is (Sa, Sb, Sc, Sd, Se, Sf);

signal CURRENT_STATE, NEXT_STATE: STATE_TYPE;

begin

-- Process to hold synchronous elements (flip-flops)
SYNCH: process(clk)
begin
if(rising_edge(clk)) then
    if(rst = '1') then
        CURRENT_STATE <= Sa;
    else
        CURRENT_STATE <= NEXT_STATE;
    end if;
end if;

CURRENT_STATE <= NEXT_STATE;
end process SYNCH;


-- Process to hold combinational logic
COMBIN: process(CURRENT_STATE, inc)
begin
case CURRENT_STATE is
when Sa =>
    outc <= "01";
    can <= '0';
    if (inc = "01") then -- 0 p
        NEXT_STATE <= Sa;
    end if;
    if (inc = "11") then --1 pound
        NEXT_STATE <= Sf;
    end if;
    if (inc = "00") then --2 pound

```



```
NEXT_STATE <= Sb;

end if;

if (inc = "10") then --50p
NEXT_STATE <= Sc;
end if;
```

```
when Sb =>

outc <= "11";
can <= '0';
NEXT_STATE <= Sf;
```

```
when Sc =>

outc <= "01";
can <= '0';
if (inc = "01") then --0p
NEXT_STATE <= Sc;
end if;

if (inc = "11") then --1 pound
NEXT_STATE <= Sd;
end if;

if (inc = "00") then --2 pound
NEXT_STATE <= Se;
end if;

if (inc = "10") then
NEXT_STATE <= Sf;
end if;
```

```
when Se =>

outc <= "11";
can <= '0';
NEXT_STATE <= Sd;
```

```
when Sd =>
  outc <= "10";

  can <= '0';
  NEXT_STATE <= Sf;

when Sf =>
  outc <= "01";

  can <= '1';
  NEXT_STATE <= Sa;

end case;
end process COMBIN;

end BEHAVIOR;
```

end of code

VHDL test bench:

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use ieee.numeric_std.all;

use ieee.std_logic_unsigned.all;


entity MOOREtb is

-- Port ( );

end MOOREtb;


architecture Behavioral of MOOREtb is

component MOORE is -- Moore machine
port(
clk, rst : in std_logic;
inc : in std_logic_Vector(1 downto 0);
outc : out std_logic_Vector(1 downto 0);
can : out std_logic
);
end component;


signal clk, rst, can : std_logic := '0';
signal outc : std_logic_Vector(1 downto 0) := "00";
signal inc : std_logic_Vector(1 downto 0) := "00";


begin

C1 : MOORE port map (clk => clk, inc => inc, outc => outc, rst => rst, can => can);


clk_process:process(clk)
begin
clk <= not clk after 10 ns; --oscillate at this specific period
```

```
end process clk_process;
```

```
control_process:process
```

```
begin
```

```
inc <= "01";
```

```
wait for 50 ns;
```

```
rst <= '1' after 10 ns ;
```

```
wait for 50 ns;
```

```
rst <= '0';
```

```
inc <= "10";
```

```
wait for 50 ns;
```

```
--£50p case
```

```
inc <= "10";
```

```
wait for 50 ns;
```

```
inc <= "01";
```

```
wait for 50 ns;
```

```
--- £50p
```

```
inc <= "10";
```

```
wait for 50 ns;
```

-----f1

inc <= "11";
wait for 50 ns;

-----f2 and 50p

inc <= "10";
wait for 50 ns;
inc <= "00";
wait for 50 ns;

-----f1.50


inc <= "10";
inc <= "11";
wait for 50 ns;
end process control_process;

end Behavioral;

End of test bench code


Simulation:

Reset case:

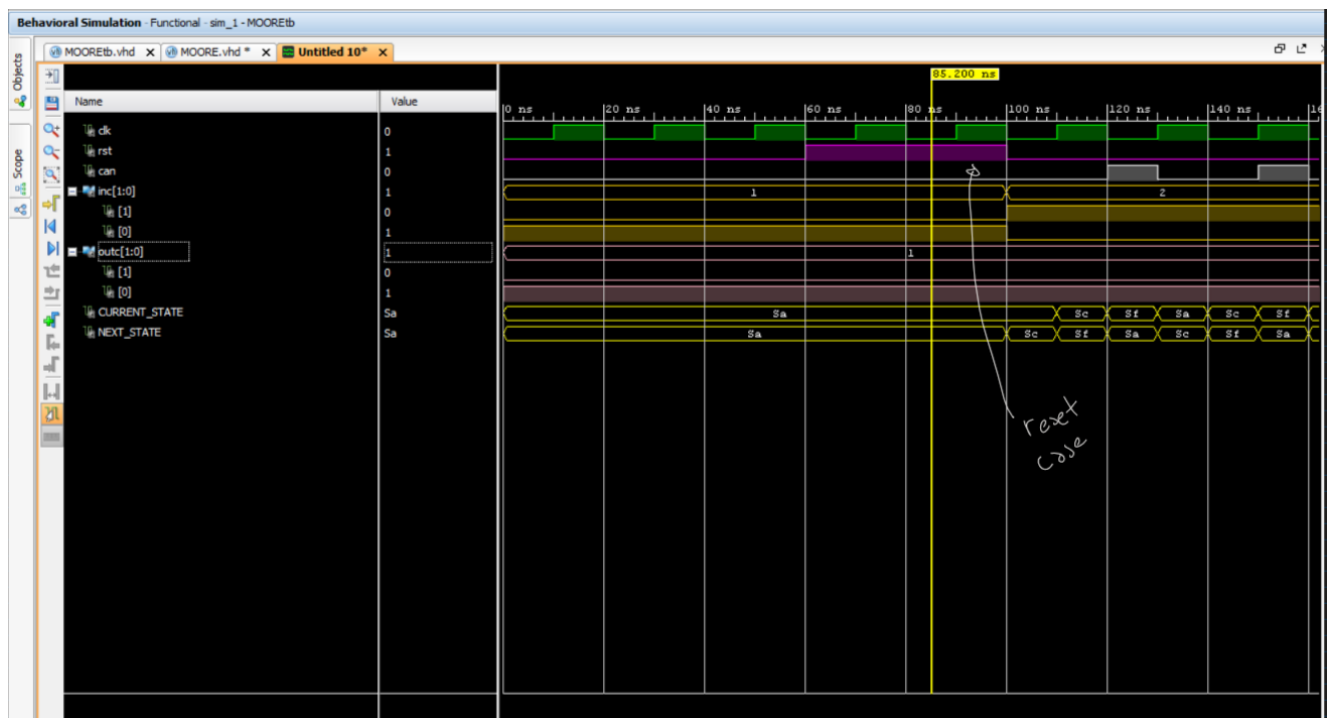


A small reset impulse is sent by the test bench as it can be seen above to fulfil the task requirement.

50p then £0 and later 50p in:

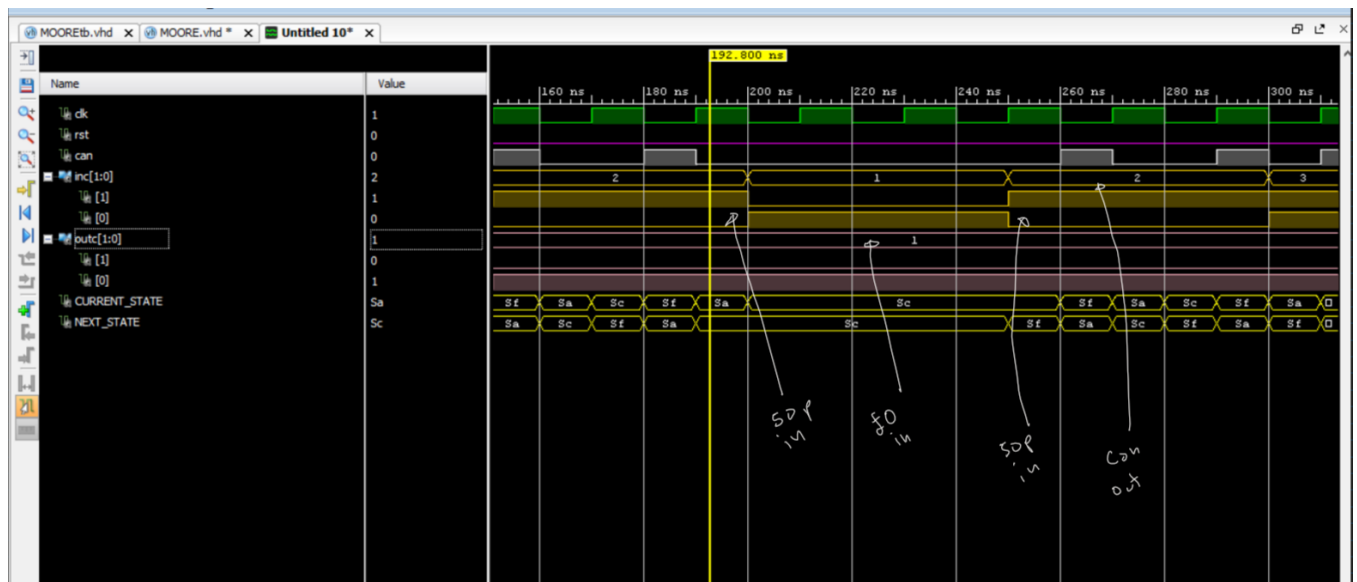


When the system has received the state changes from `Sa` to `Sc` and wait in there while £0 has been inserted, later when 50p has been inserted the the state changes from `Sc` to `Sf` and it returns to the initial state `Sa`. We get no change. This waveform confirms the correct state jumps.

Just £1 pound in and later 50p in case:

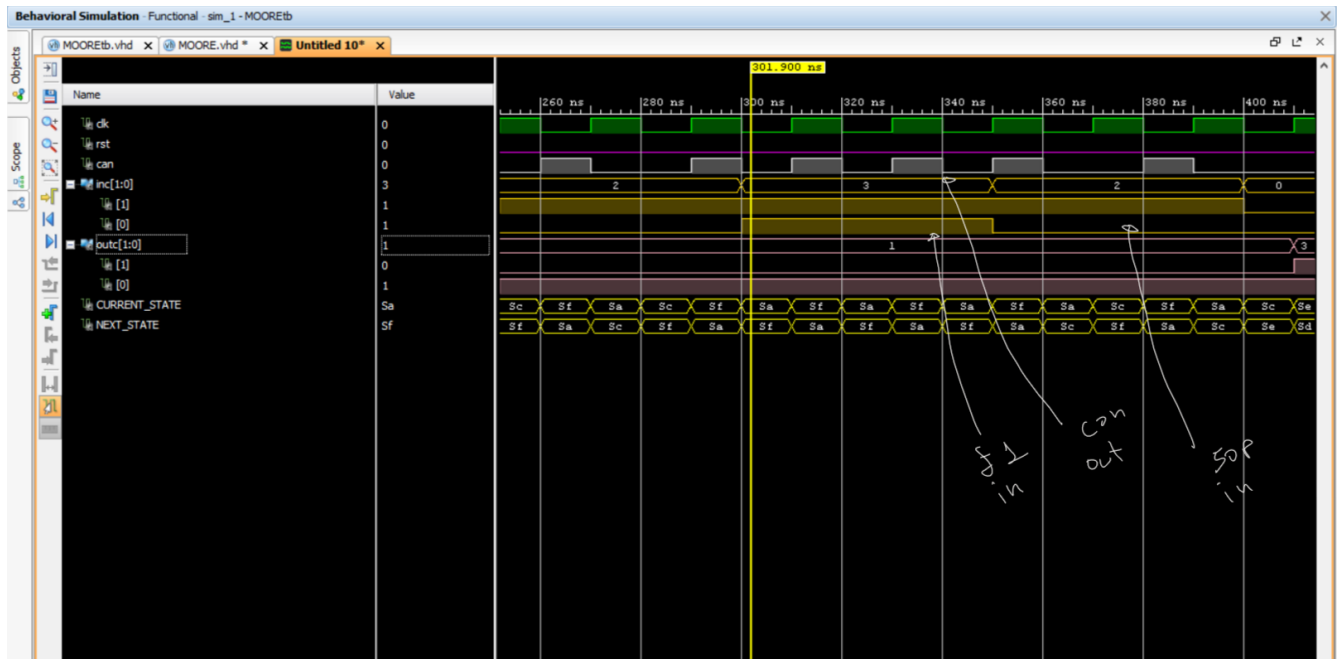


When £1 pound is inserted, the machine goes from `Sa` directly to `Sf`. This where a can is dispensed and it returns to the initial state `Sa` and later goes to `Sc` as 50p is inserted.

50p in then £2 in case:

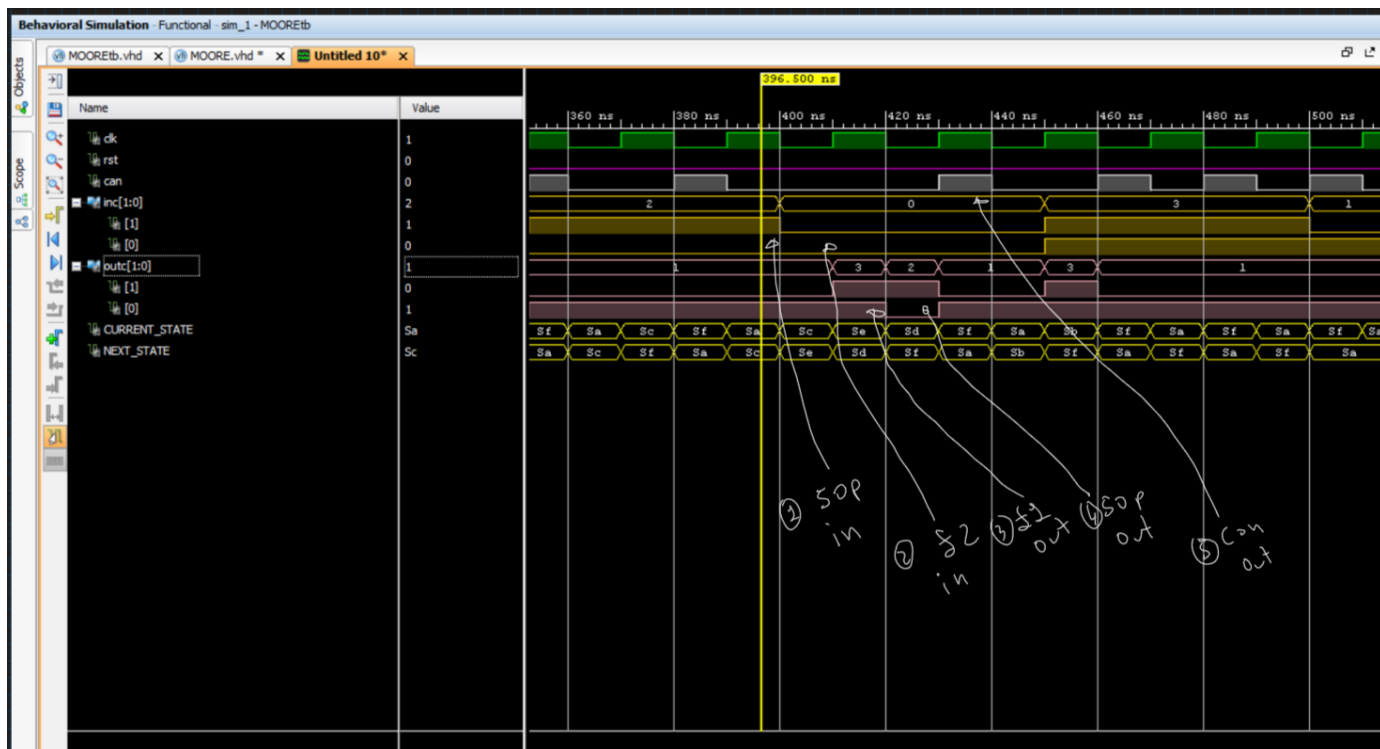

Just 50p case:

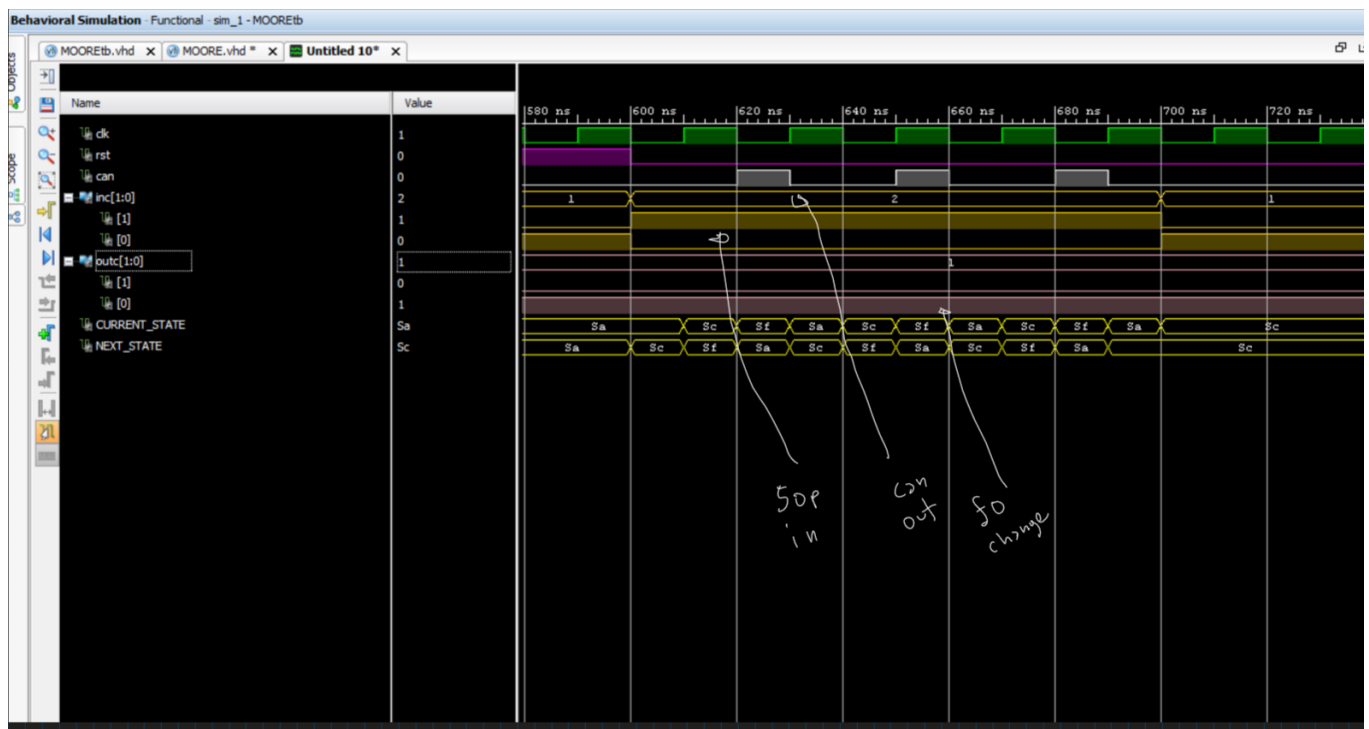

50p and £1 case:

